

```

`timescale 1ns / 1ps

/*****
*****
*
*  Module:  Stopwatch
*
*  Author:  Eric Christie
*  Class:   ECEN 220, Section 1, Winter 2021
*  Date:    3/9/21
*
*  Description:  Instances the Mod_Counter
module to create a 4-digit stopwatch based
on a 100 Hz counter
*
*
*****
*****/

`default_nettype none

module Stopwatch(
    input wire logic clk, reset, run,
    output logic [3:0] digit0, digit1,

```

```
digit2, digit3);
```

```
    logic timer_runover;
```

```
    logic [19:0] timer_out;
```

```
    logic [3:0] runover;
```

```
    //module      Mod_Value, WID      clk,  
reset, increment, rolling_over, count (WID)
```

```
    Mod_Counter #(1000000, 20) Timer(clk,  
reset, run, timer_runover, timer_out);
```

```
    Mod_Counter #(10, 4) D0(clk, reset,  
timer_runover, runover[0], digit0);
```

```
    Mod_Counter #(10, 4) D1(clk, reset,  
runover[0], runover[1], digit1);
```

```
    Mod_Counter #(10, 4) D2(clk, reset,  
runover[1], runover[2], digit2);
```

```
    Mod_Counter #(6, 4) D3(clk, reset,  
runover[2], runover[3], digit3);
```

```
endmodule
```