```
`timescale 1ns / 1ps
/**********
********
\star
* Module: debounce top
\star
 Author: Eric Christie
* Class: ECEN 220, Section 1, Winter 2021
* Date: 3/16/21
*
* Description: Synchronizer fed to
debouncer to One Shot to the final counter
                Also has an
un-debounced line from the synchronizer
for contrast
**********
**********
`default nettype none
module debounce top(
   input wire logic clk, btnu, btnc,
   output logic [3:0] anode,
   output logic [7:0] segment);
```

```
logic FF1, FF2; //synchronizer flip
flops
    logic debounced; //output from
debouncer
    logic dOS FF, dOS, rOS_FF, rOS; //One
shot flip-flop and output for debouncer
and raw
    logic [7:0] debCount, rawCount;
//counters
    //Synchronizer
    always ff @(posedge clk) begin
        FF1 <= btnc;
        FF2 <= FF1;
    end
    //debouncer - clk, reset, noisy,
debounced (output)
    debounce db(clk, btnu, FF2, debounced);
    //One Shot
    always_ff @(posedge clk) dOS FF <=
debounced;
```

```
assign dOS = !dOS FF && debounced;
    //debounced counter
    always ff @(posedge clk) begin
        if(btnu) debCount <= 0;</pre>
        else if (dOS) debCount <= debCount
+1;
    end
    //non-debounced One Shot and Counter
    always ff @(posedge clk) rOS FF <= FF2;
    assign rOS = !rOS FF \&\& FF2;
    always ff @(posedge clk) begin
        if(btnu) rawCount <= 0;</pre>
        else if(rOS) rawCount <= rawCount</pre>
+1;
    end
    //Seven Segment Display clk, reset,
```

dataIn, digitDisplay, digitPoint, anode,

segment
 SevenSegmentControl SSC(clk, btnu,
{rawCount, debCount}, 4'b1111, 4'b0000,
anode, segment);

endmodule